

Assignment 4.1

16-bit ALU


Introduction: -

ALU_TOP is the fundamental building block of the processor, which is responsible for carrying out different functions: -

- **Arithmetic** functions through **ARITHMETIC_UNIT** block.
- **Logic** functions through **LOGIC_UNIT** block.
- **Shift** functions through **SHIFT_UNIT** block.
- **Comparison** functions through **CMP_UNIT** block.

And **Decoder Unit** responsible for enable which Function to operate according to the highest Most significant **2-bit** of the ALU_FUNC control bus **ALU_FUNC [3:2]**.

Block Diagram

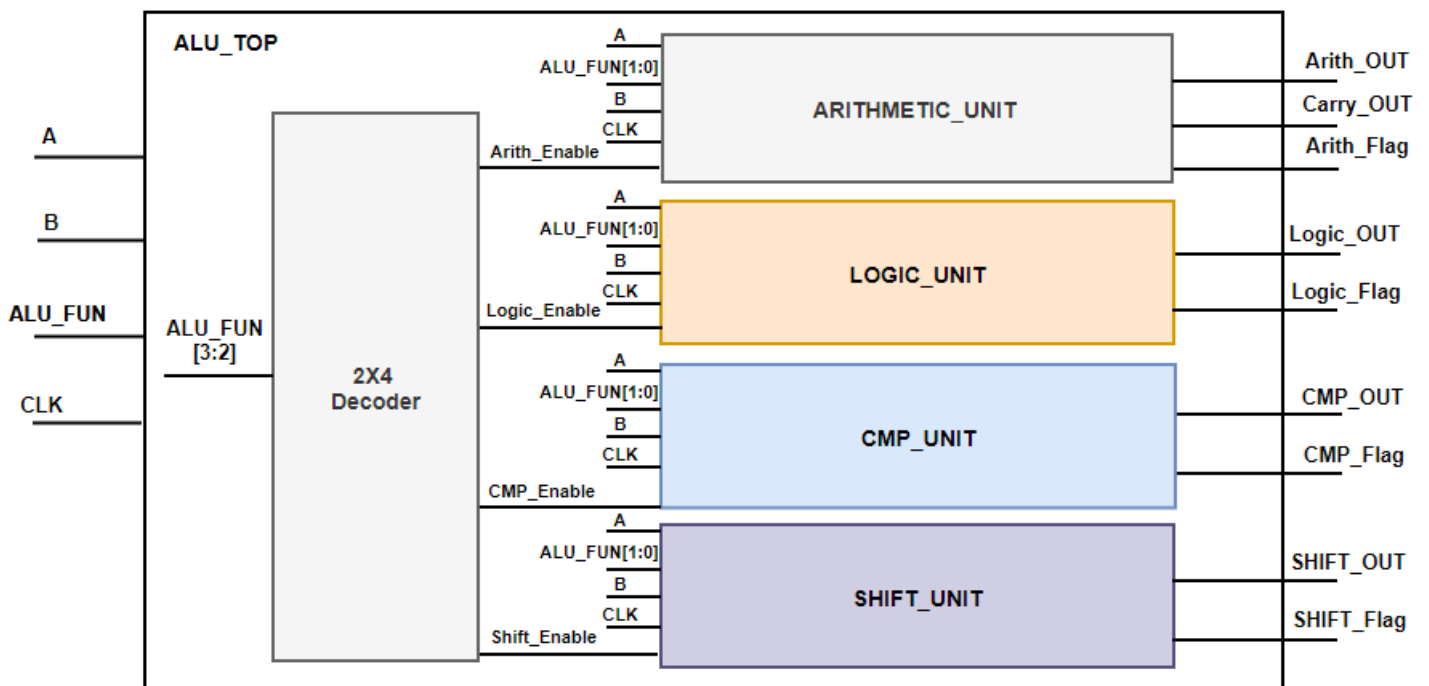

TOP Module (ALU_TOP) Port Description:

Signal Name	Width (bits)
A	parameterized
B	parameterized
ALU_FUNC	4
CLK	1
Arith_OUT	parameterized
Carry_OUT	1
Arith_Flag	1
Logic_OUT	parameterized
Logic_Flag	1
CMP_OUT	parameterized
CMP_Flag	1
SHIFT_OUT	parameterized
SHIFT_Flag	1

Specifications: -

- All Outputs are registered.
- All registers are cleared using **Asynchronous active low reset**
- **Arith_flag** is activated "High" only when ALU performs one of the arithmetic operations (Addition, Subtraction, Multiplication, division), otherwise "LOW"
- **Logic_flag** is activated "High" only when ALU performs one of the Boolean operations (AND, OR, NAND, NOR), otherwise "LOW"
- **CMP_flag** is activated "High" only when ALU performs one of the Comparison operations (Equal, Greater than, less than) or NOP, otherwise "LOW"
- **Shift_flag** is activated "High" only when ALU performs one of the shifting operations (shift right, shift left), otherwise "LOW"
- The ALU function is carried out according to the value of the **ALU_FUN** input signal stated in the following table

ALU_FUN Table

ALU_FUN	Operation	ALU_OUT
0000	Arithmetic : Addition	
0001	Arithmetic : Subtraction	
0010	Arithmetic : Multiplication	
0011	Arithmetic : Division	
0100	Logic : AND	
0101	Logic : OR	
0110	Logic : NAND	
0111	Logic : NOR	
1000	NOP	Equal to 0
1001	CMP: A = B	Equal to 1
1010	CMP: A > B	Equal to 2
1011	CMP: A < B	Equal to 3
1100	SHIFT: A >> 1	
1101	SHIFT: A << 1	
1110	SHIFT: B >> 1	
1111	SHIFT: B << 1	

Hint: Use Case statement to describe the behavior of this table and use default case if needed.

Hint: You can use if statement inside case branches.

Note: **Arith_Enable**, **Logic_Enable**, **SHIFT_Enable** and **CMP_Enable** are called block enable which responsible for enabling the function of the block or not.

Decoder Truth Table

ALU_FUNC[3:2]	Arith_En	Logic_En	CMP_EN	SHIFT_EN
00	1	0	0	0
01	0	1	0	0
10	0	0	1	0

11	0	0	0	1
----	---	---	---	---

Hint: How to use the enable signal inside the code of each block.

```

always @(*)
begin
  if(Arith_Enable)
  begin
    case(ALU_FUN)
      2'b00 : {ALU_Carry, ALU_Arith } = A + B ;
      .....
    endcase
  end
else
  begin
    ALU_Arith = 16'b0 ;
  End
End

```

Requirements: -

- Write a Verilog Codes of the following **6 modules**
 - **ARITHMETIC_UNIT**
 - **LOGIC_UNIT.**
 - **SHIFT_UNIT**
 - **CMP_UNIT**
 - **Decoder Unit**
 - **ALU_TOP**
- Write a testbench to test all the ALU functions with operating clock frequency 100 KHz with duty cycle 40% low and 60% high

